

(3 Hours)

[Total Marks : 80

- N.B. :** (1) Question No. 1 is compulsory.
 (2) Attempt any 3 questions from Q.2 to Q.6.
 (3) Figures to the right in the bracket indicate full marks.
 (4) Assume suitable data if necessary.

- | | | | |
|----|----|---|----|
| 1. | a) | State basic theorems of Boolean algebra. | 5 |
| | b) | Compare Mealy and Moore machine | 5 |
| | c) | Define Noise Margin, Propagation delay, Power Dissipation | 5 |
| | d) | Design a full adder using half adders and logic Gates | 5 |
| 2. | a) | Prove that NAND and NOR Gates are universal Gates | 10 |
| | b) | Design a 2-bit comparator and implement using logic Gates | 10 |
| 3. | a) | Design a 4 bit Binary to Grey code converter. | 10 |
| | b) | Implement the given function using single 4:1 Multiplexer and few logic gates: $F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 10, 12, 13, 15)$ | 10 |
| 4. | a) | What is a universal shift register? Explain its various modes of operation | 10 |
| | b) | Write a VHDL program to design a 3:8 Decoder. | 10 |
| 5. | a) | Minimize the following expression using Quine McClusky Technique
$F(A,B,C,D) = \sum m(0,1,2,3,5,7,9,11)$ | 10 |
| | b) | Convert JK FF to T FF and JK FF to D FF | 10 |
| 6. | a) | Explain the working of 3-bit asynchronous counter with proper timing diagram. | 10 |
| | b) | Write a note on CPLDs. | 10 |
