

- Attempt any 4 questions:

- (a) Give ideal characteristics of op-amp and give their practical values. [05]
  - (b) Compare linear and switching voltage regulator. [05]
  - (c) Design a circuit for  $V_O = V_1 + V_2$  using single op-amp and few resistors. [05]
  - (d) What are the advantages of switch capacitor filters? [05]
  - (e) Explain op-amp as window detector. [05]
- 
- (a) With the help of a neat diagram and voltage transfer characteristics explain the working of an inverting Schmitt trigger. Derive the expressions for its threshold levels. [10]
  - (b) Draw a neat circuit diagram of a Wien bridge oscillator using op-amp. Derive its frequency of oscillation. What are the values of  $R$  and  $C$  for frequency of oscillation to be 965 Hz? [10]
- 
- (a) Draw the circuit diagram of a square and triangular waveform generator using op-amp and explain its working with the help of waveforms. [10]
  - (b) The circuit given in Fig. 3(b) is similar to that of internal diagram of IC555 with slight modifications in the internal resistances to value  $2R$ . Analyse this circuit and draw the waveforms at output terminal  $v_{out}$  and across the capacitor  $C$ . Comment on the duty cycle of output waveform when i)  $R_A$  is less than  $R_B$ , ii)  $R_A$  is equal to  $R_B$ , and iii)  $R_A$  is greater than  $R_B$ . [10]

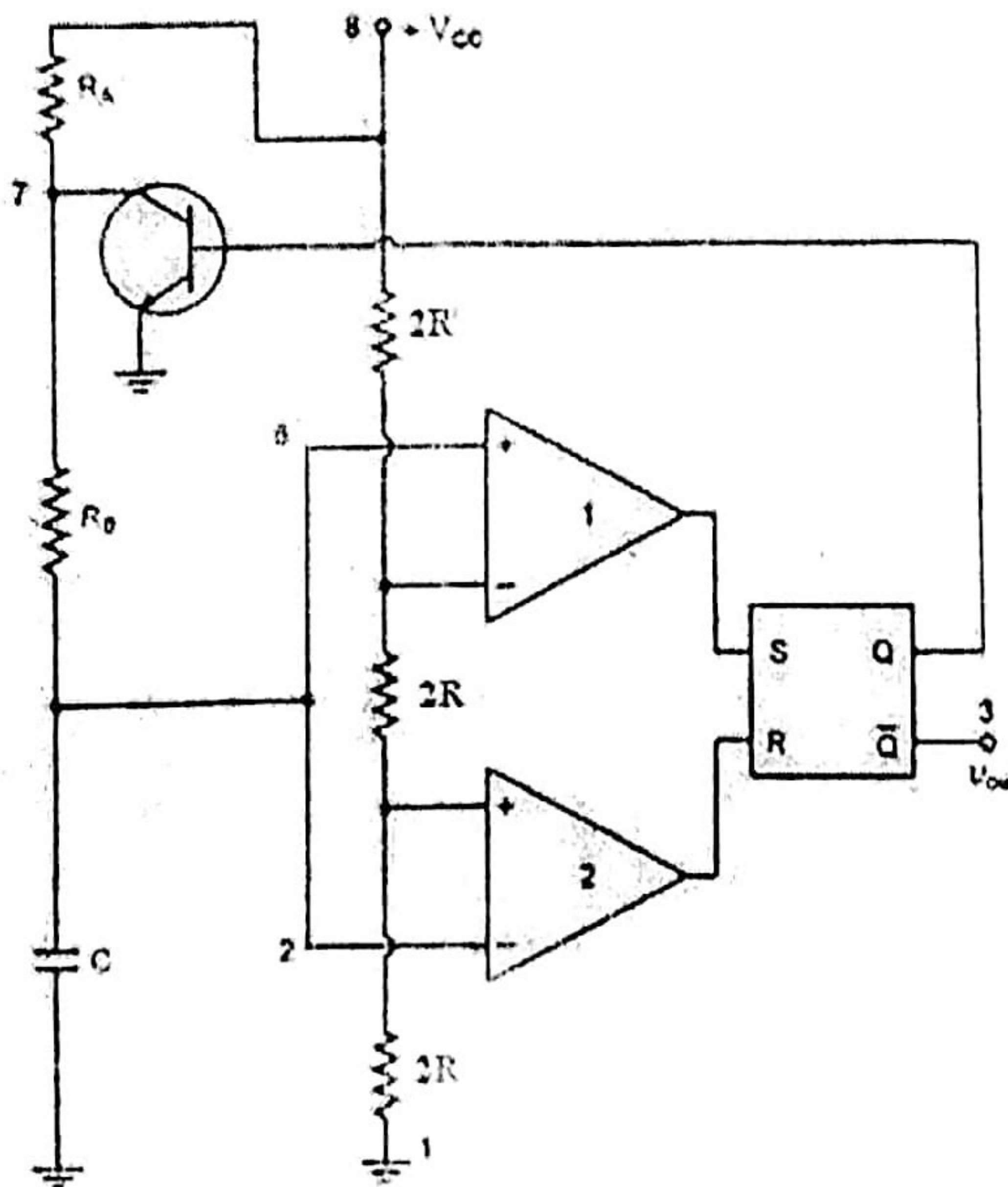


Fig. 3(b)



- Q.4 (a) Design a second order Butterworth high pass filter for cut off frequency of kHz and pass-band gain of  $AF=2$ .  
(b) With a neat circuit derive an expression for the output of an instrumentation amplifier.
- Q.5 (a) With neat circuit explain R/2R ladder digital to analog converter.  
(b) With the help of a functional block diagram explain the working of voltage regulator LM317 to give an output voltage variable from 6 V to 12 V to handle maximum load current of 500 mA.
- Q.6 Short notes on: (Attempt any four)  
(a) Effect of swamping resistor.  
(b) Current fold-back protection circuit in voltage regulator.  
(c) Voltage to Current converter.  
(d) Peak detector circuit.  
(e) Working of PLL IC 565.

\*\*\*\*\*