

Time: 3 Hours


Marks: 80

- Question no.1 is compulsory
- Attempt any three questions out of remaining questions
- Assume suitable data if required
- Figures to the right indicate marks.

No. 1) Solve the following

[20]

 a) Calculate the voltage at the output node  $V_o$  if  $V_{DD}=5V$  and  $V_{th}=1.5V$



- b) Draw and Explain Clocked SR latch using static CMOS design style.
- c) Draw layout diagram of static CMOS inverter based on lambda design rules.
- d) Draw VTC of static CMOS inverter and show operating regions of nMOS and pMOS transistors on it.
- e) Explain short channel effects (any two).

No. 2)

a) Explain in detail the fabrication process steps for a CMOS inverter using n-well process with the help of cross sectional view for each step. [10]

b) Implement a two input XOR gate using

- (i) static CMOS logic
- (ii) Dynamic logic
- (iii) Transmission gate
- (iv) Pseudo NMOS logic

[10]

No. 3)

a) Derive an expression for the inverter threshold voltage (switching voltage) of a CMOS inverter. Calculate the (W/L) ratios of the NMOS and PMOS transistor in the CMOS inverter circuit with the following parameters:

$$V_{DD} = 3V \quad V_{t0,n} = 0.6V \quad V_{t0,p} = -0.8V \quad V_{TH} = 1.5V$$

$$\mu_n C_{ox} = 60 \mu A/V^2 \quad \mu_p C_{ox} = 20 \mu A/V^2$$

[10]

b) Draw schematic diagram of six transistor SRAM cell and explain its Read and Write operations.

[10]



Q. No. 4)

- a) What is scaling. Compare constant field scaling with constant voltage state advantages and limitations in both the methods.
- b) Design a 4- bit CLA adder using dynamic NMOS logic. Compare circuit with respect to a 4 bit ripple carry adder.

Q. No. 5)

- a) Draw the CMOS circuit for  $Y = \overline{A + BC(D + E) + F}$  and find CMOS inverter circuit for simultaneous switching of all inputs,  $(W/L) = 15$  for all pMOS transistors and  $(W/L) = 10$  for all nMOS transistors.
- b) Explain in detail static and dynamic power dissipation. What are the components which make power dissipation in CMOS circuit?

Q. No.6) Explain any 2 of the following

- a. 4 bit Array Multiplier
- b. Interconnect Delay model
- c. 3-T DRAM