

CTL

QP Code : 30754

(3 Hours)

[ Total Marks : 80

- N.B.:
- (1) Attempt questions No. 1 and any 3 from remaining questions. In all 4 questions are to be attempted.
  - (2) All sub-questions of the same question should be answered at one place only in their serial orders, and not scattered.
  - (3) Assume suitable data with justification if missing.

1. (a) Determine Y - parameters for the network shown in fig 1 (a) 5

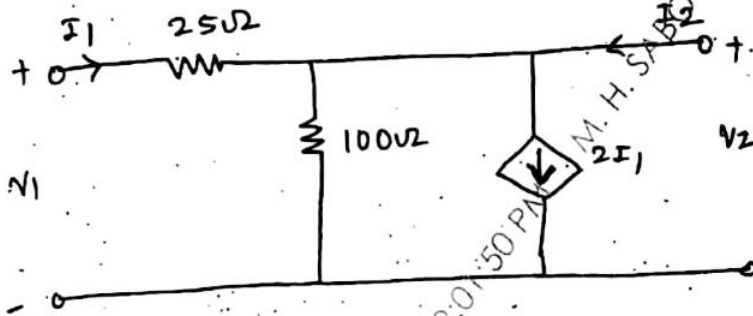


Fig 1 (a)

- (b) Test if  $F(s) = s^4 + s^3 + 5s^2 + 3s + 4$  is a Hurwitz polynomial. 5
- (c) Two coils connected in series have self inductance 80 mH & 20 mH respectively 5  
The total inductance of the circuit is found to 140 mH. Determine the
  - (i) mutual inductance between two coils and
  - (ii) The coefficient of coupling
- (d) Synthesize the following function into a network. 5

$$z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1} \text{ using cauer -1 form.}$$

[ TURN OVER ]

2. (a) Find the Thevenin's equivalent across the terminals XY for the circuit shown in fig 2 (a)

10

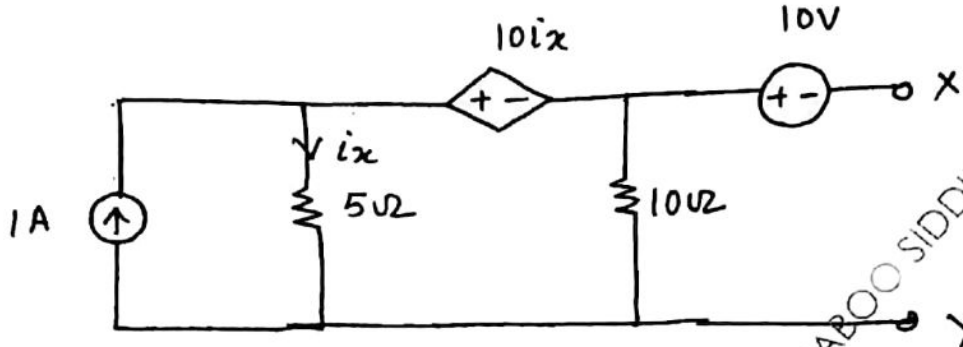


Fig 2(a)

- (b) Determine the node voltage at node (1) & (2) of the Network Shown in fig 2(b) by using nodal analysis.

5

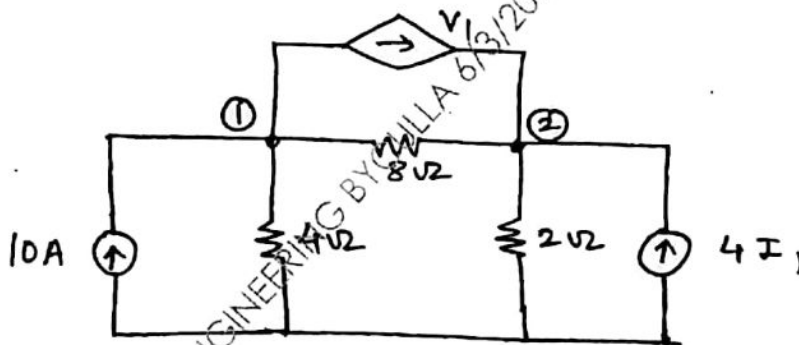


Fig 2(b)

- (c) Test Whether

$$F(s) = \frac{s(s+3)(s+5)}{(s+1)(s+4)}$$

is a positive real function.

5

- (a) Synthesize the driving point function using Foster -I and Foster -II form. 10

$$z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

- (b) State and prove Initial value theorem. 5

- (c) A Transmission line has distributed parameters  $R=6 \text{ Ohms / km}$ ,  $L=2.2 \text{ mH/km}$ ,  $C=0.005 \text{ } \mu\text{F /km}$  &  $G=0.005 \text{ } \mu\text{ mho/km}$ . 5  
Determine characteristics impedance and propagation constant at 1KHz frequency.

- i. (a) Find ABCD parameters for the two port Network shown in fig 4 (a). 10

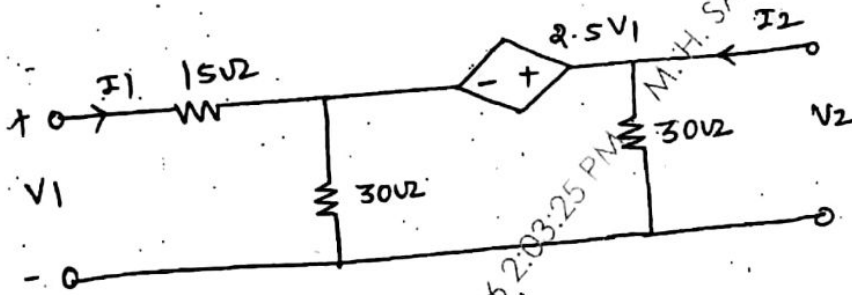


Fig 4(a)

- (b) Find the Network functions  $\frac{V_2}{I_1}$ ,  $\frac{V_2}{I_1}$ ,  $\frac{V_2}{V_1}$  for the network shown in fig 4 (b) 5

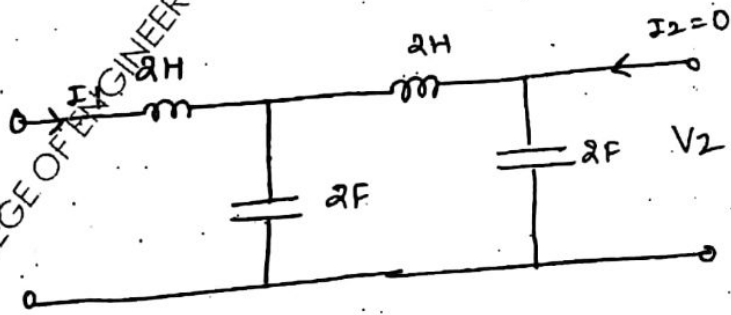


Fig 4(b)

[ TURN OVER ]

- (c) A Transmission line has a characteristics impedance of  $50 + j 100 \Omega$  and is terminated in a load impedance of  $73 - j 42.5 \Omega$ . Calculate
- The reflection coefficient.
  - The standing wave ratio.

5. (a) The Network shown in fig 5 (a), switch K is closed at  $t = 0$ , Assume all initial conditions as zero. Find  $i$ ,  $\frac{di}{dt}$  &  $\frac{d^2i}{dt^2}$  at  $t = 0^+$

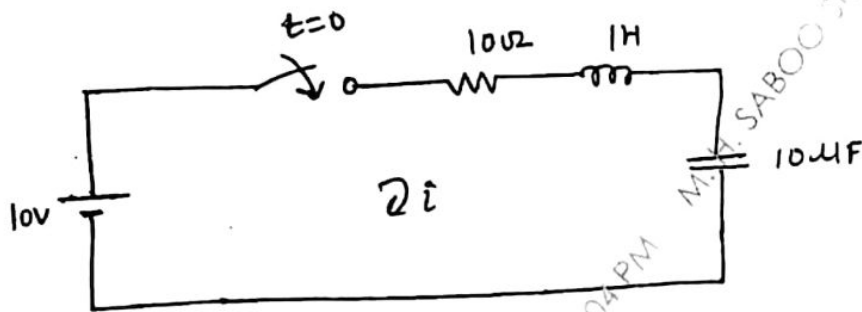


Fig 5(a)

- (b) Write the KVL equations in standard form for the N/W shown in fig 5(b)

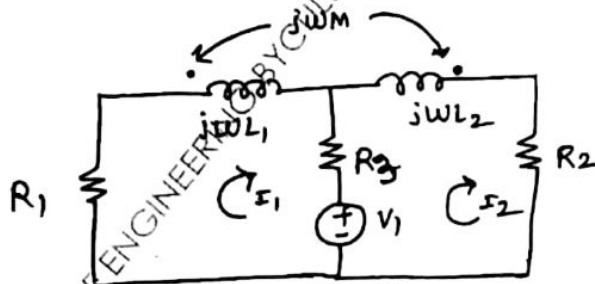


Fig 5(b)

[ TURN OVER ]

(c) Find poles and zero of the Impedance  $Z(s)$  for the Network Shown in fig 5 (c)

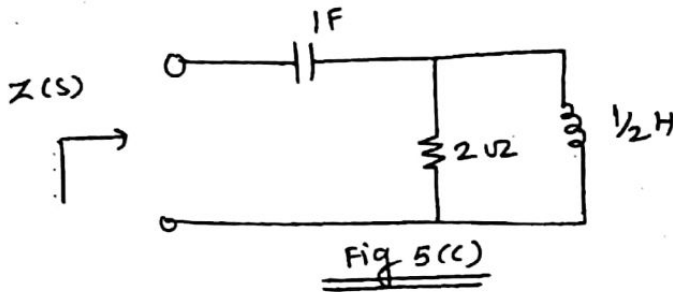


Fig 5(c)

6. (a) Why is the Impedance matching required? Draw the following normalized quantities on the smith chart. 10
- |                       |                     |
|-----------------------|---------------------|
| (i) $(3+i3) \Omega$   | (ii) $(1.0) \Omega$ |
| (iii) $(2-j1) \Omega$ | (i) $j 1.0 \Omega$  |
- (b) Write short note on : 5  
Time domain analysis using Laplace Transform.
- (c) Define the following terms 5
- (i) Phase Velocity
  - (ii) Characteristic impedance
  - (iii) Reflection coefficients

Course: SE (all Branches)

QP Code 30754

Correction

---

Q.No.2 (b)

In Q.2 (b),  
Replace (b)  $\uparrow 4I_1$  by  $\diamond \uparrow 4I_1$

Almp  
03/6/16

Q. No. 6 (a) (i)

Replace  $(3+i3)$  by  $(3+j3)$

---

Date and Time 03/06/2016 04:18 PM