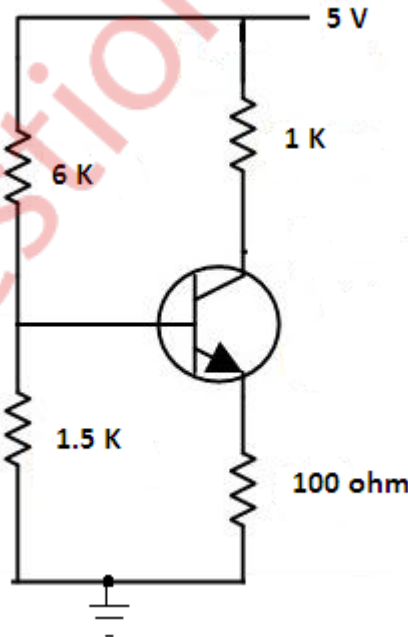


(3 Hours)


Maximum Marks 80

- N.B: (1) Question No.1 is compulsory.
 (2) Solve any three out of remaining question.
 (3) Assume suitable data if necessary.

Que-1	Solve any Four	Marks
a	What happens when pn junction diode is made forward bias, explain considering any suitable application.	5
b	Explain how CC configuration of BJT gives voltage gain less than 1	5
c	Explain with the help of construction that MOSFET gives more Input resistance than JFET	5
d	What is varactor Diode, also state its applications.	5
e	Compare C, L and LC filters.	5
Que-2a	Draw Energy band diagram of pn junction diode under i) Zero Bias ii) Forward bias and iii) Reverse Bias	10
Que-2b	For the given circuit find Steady State DC Parameters I_{cq} and V_{ceq} Given $\beta = 100$ and $V_{BE} = 0.7 \text{ V}$, also state in which region the circuit is working.	10



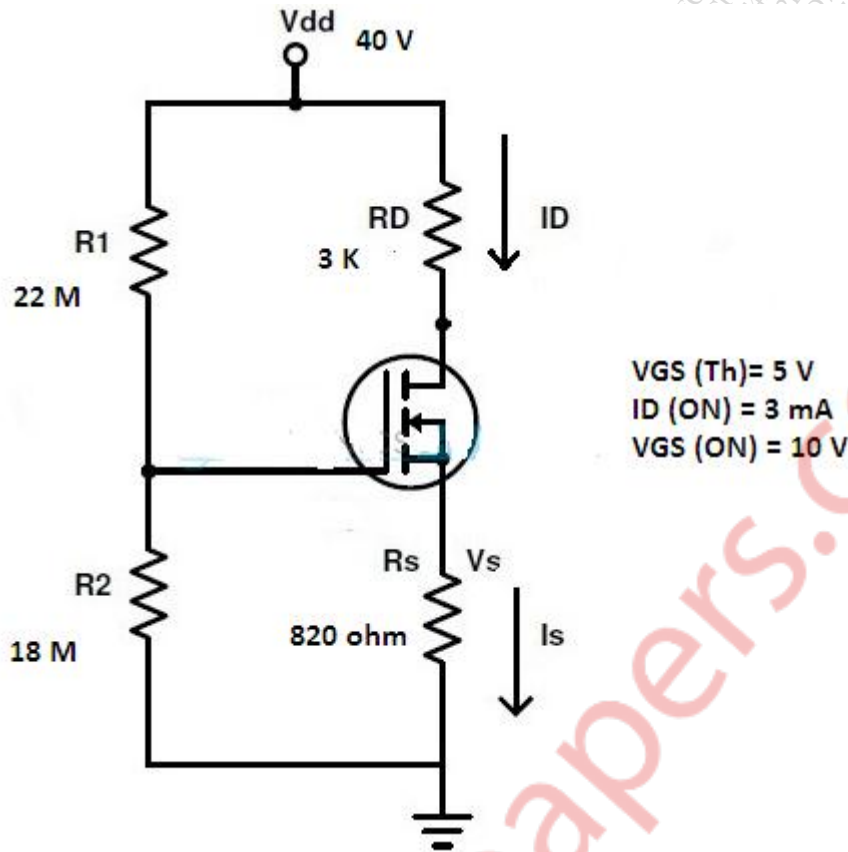Que-3a For the given MOSFET amplifier, Determine I_{DQ} , V_{GSQ} and V_{DS} . 10



Que-3b Explain working principle, characteristics and applications of Photodiode. 10

Que-4a What is the need of Filters, Explain L filter circuit? 10

Que-4b For the voltage divider biased BJT amplifier without bypass capacitor circuit derive equation of Input resistance, Voltage gain, current gain and output resistance. 10

Que-5a Design Single Stage CE amplifier for the given specifications 15
 $A_v \geq 100$, $S = 10$, $V_o = 3\text{ V}$, $f_L = 20\text{ HZ}$, use transistor BC 147 B
 Use coupling and bypass capacitor as $C_1 = C_2 = 10\text{ }\mu\text{F}$ and $C_E = 100\text{ }\mu\text{F}$.

Que-5b What is Clamping circuit, explain with neat Input and output waveforms for negative Clamping circuit. 05

Que-6a For the voltage divider biased E MOSFET circuit derive equation of Input Resistance, Voltage gain and output resistance. 10

Que-6b Derive equation of Input resistance, Current gain and Voltage gain for CC amplifier. 10

DBEC DATA SHEET

Transistor type	P _{dmax} @ 25°C Watts	I _{cmax} Amps	V _{CE} ^(sat) volts	V _{CE0} volts	V _{CE0} (Sus) volts	V _{CE0} (Sus) d.c. volts	V _{CE0} (Sus) d.c. volts	V _{CE0} (Sus) d.c. volts	V _{BE0} volts	T _j max °C	D.C. current gain		Signal typ.	h _{FE} max.	V _{BE} max.	θ _{JA} °C/W	Derate above 25°C W/°C
											min	typ.					
2N 3055	115-5	15-0	1-1	100	60	70	90	7	200	20	50	70	15	50	1-8	1-5	0-7
ECN 055	50-0	5-0	1-0	60	50	55	60	5	200	25	50	100	25	75	1-5	3-5	0-4
ECN 149	30-0	4-0	1-0	50	40	—	—	8	150	30	50	110	33	60	1-2	4-0	0-3
ECN 100	5-0	0-7	0-6	70	60	65	—	6	200	50	90	280	50	90	0-9	35	0-05
BC147A	0-25	0-1	0-25	50	45	50	—	6	125	115	180	220	125	220	0-9	—	—
2N 525(PNP)	0-225	0-5	0-25	85	30	—	—	—	100	35	—	65	—	45	—	—	—
BC147B	0-25	0-1	0-25	50	45	50	—	6	125	200	290	450	240	330	0-9	—	—

BFW 11-JFET MUTUAL CHARACTERISTICS

-V _{GS} volts	I _{DS} max. mA	I _{DS} typ. mA	I _{DS} min. mA	I _{oss}	T _j max.	P _d max. @25°C	V _{GS} max. Volts	V _{DS} max. Volts	V _{DS} max. Volts	h _{FE} (typical)	r _d	Derate above 25°C	θ _{JO}
10	9-0	8-3	7-6	6-8	6-1	5-4	4-2	3-1	2-2	2-0	1-1	0-5	0-0
7-0	6-0	5-4	4-6	4-0	3-3	2-7	1-7	0-8	0-2	0-0	0-0	0-0	0-0
4-0	3-0	2-2	1-6	1-0	0-5	0-0	0-0	0-0	0-0	0-0	0-0	0-0	0-0

N-Channel JFET

Type	V _{GS} max. Volts	V _{DS} max. Volts	V _{GS} max. Volts	V _{DS} max. Volts	P _d max. @25°C	T _j max.	I _{oss}	h _{FE} (typical)	-V _p Volts	r _d	Derate above 25°C	θ _{JO}
2N3822	50	50	50	50	300 mW	175°C	2 mA	3000 μΩ	6	50 KΩ	2 mW/°C	0-59°C/mW
BFW 11 (typical)	30	30	30	30	300 mW	200°C	7 mA	5600 μΩ	2-5	50 KΩ	—	0-59°C/mW