

(3 Hours)

[Total Marks: 80]

N.B: (1) Question No.1 is compulsory.

(2) Attempt any three questions from remaining questions.

(3) Assume suitable data if required.

(4) Attempt every question in a group and not randomly.

1. (a) Check for Hurwitz polynomial

(20)

$$Q(S) = S^5 + S^3 + S^1$$

$$Q(S) = S^4 + 6S^3 + 8S^2 + 10$$

- (b) Obtain s-domain (Laplace Transform) equivalent circuit diagram of an inductor and capacitor with initial conditions.

(c) What are conditions for rational function $F(S)$ with real coefficient to be p.r.f?

(d) Explain Y-parameter in terms of Z-parameter.

2. (a) Realise the following function in Foster-I and Foster-II forms.

(20)


$$Z(S) = \frac{3(S+2)(S+4)}{S(S+3)}$$

- (b) Realise the following function in Cauer-I and Cauer-II forms.


$$Z(S) = \frac{(S+1)(S+3)}{S^2+2S}$$

3. (a) Obtain hybrid parameter of the inter connected network.


(20)

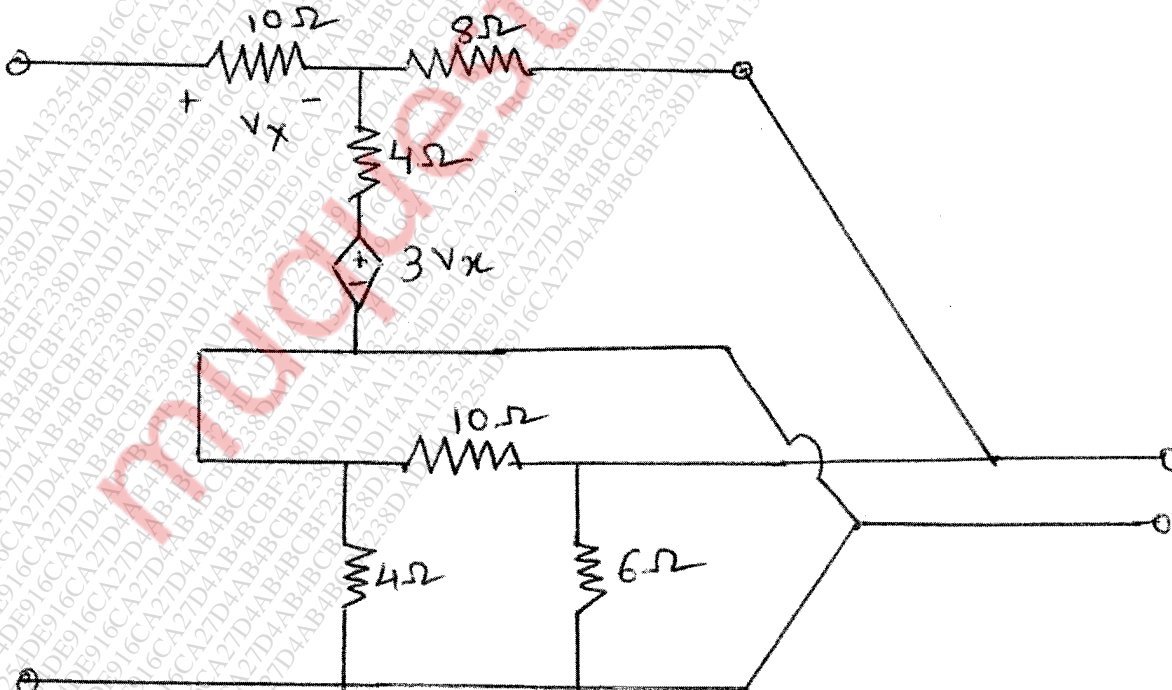

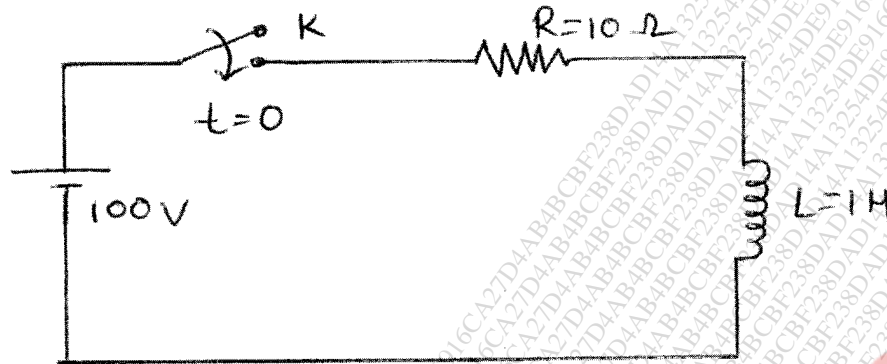(b) The switch is closed at $t=0$, find values of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0+$. Assume all initial current of inductor to be zero for circuit



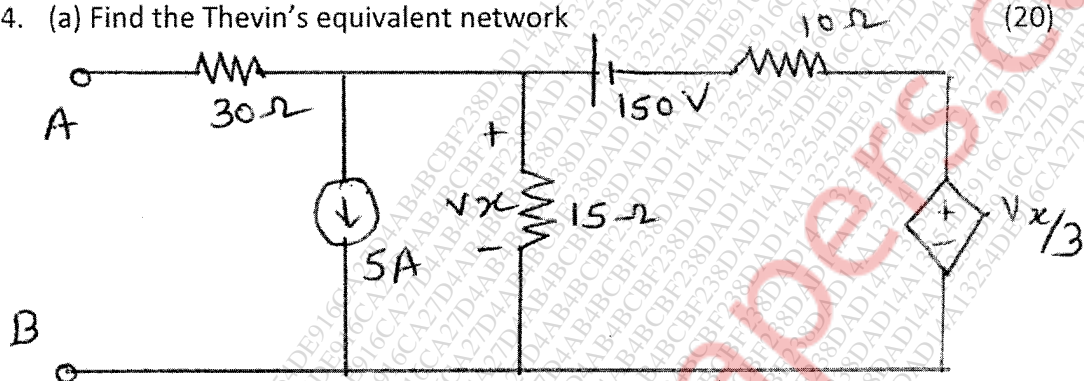4. (a) Find the Thevin's equivalent network




(b) Obtain $i(t)$ for $t > 0$



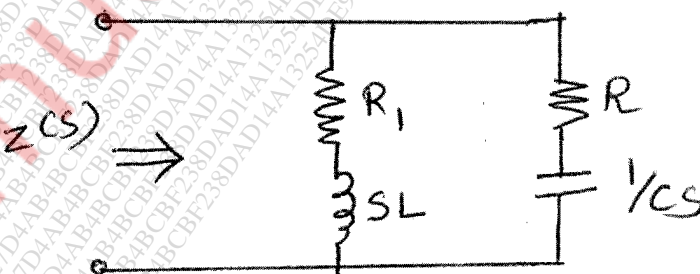
5. (a) The poles and zeros of the network shown below are as follows:

Poles at $-1+j\sqrt{5}$, $-1-j\sqrt{5}$, zeros at $-1, -3$ and the scale factor is K . If $Z(0) = 1$. Find the values of R, R_1, L and C .



TURN OVER

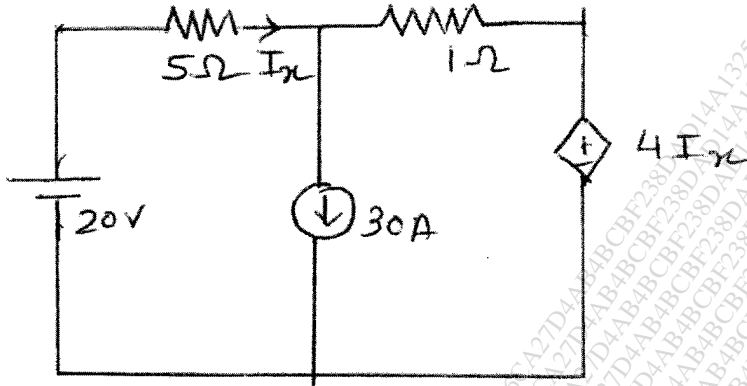(b) Find the current I_x using superposition theorem.



6. (a) Check whether the following functions are prf or not:- (20)

$$F(S) = \frac{2S^4 + 7S^3 + 11S^2 + 12S + 4}{S^4 + 5S^3 + 9S^2 + 11S + 6}$$

(b) Find Voltage across 5Ω resistor using mesh Analysis.

